



# United International University (UIU)

Department of Computer Science and Engineering  
CSE 1325/225: DIGITAL LOGIC DESIGN, Midterm Fall 2021

Total Marks: 30 Duration: 1 hour 45 Min

## Answer Any Two Questions from Q1 to Q3

1.	<p>a) Represent the numbers <math>(911)_{10}</math> and <math>(119)_{10}</math> in BCD, and then show the steps necessary to form their sum.</p> <p>b) Determine the radix <math>r</math> in the following case: <math>(911)_r = (1101)_{10}</math></p>	[3]  [3]
2.	<p>a) Simplify the following Boolean Expression (using algebraic manipulation) to an expression containing a minimum number of literals: <math>A + B(C + \overline{A + C})</math> <span style="color: blue;"><math>A + B</math></span></p> <p>b) Convert the following expression into both canonical SoP and canonical PoS forms: <math>G(L, M, N) = (L + MN)(M + LN)</math></p>	[2]  [4]
3.	<p>a) Prove that the following Boolean Function is self-dual. Then find its complement. <math>H(P, Q, R) = (\overline{P} + \overline{Q})(\overline{Q} + \overline{R})(\overline{R} + \overline{P})</math></p> <p>b) Reduce the following Boolean Expression (using algebraic manipulation) to three literals: <math>\overline{(\overline{X} \overline{Y} + Z)} + Z + XY + WZ</math> <span style="color: blue;"><math>Z + XY</math></span></p>	[3]  [3]

## Answer Any Two Questions from Q4 to Q6

4.	<p>Optimize the following Boolean functions <math>F</math> together with the don't-care conditions <math>d</math>. Find all prime implicants and essential prime implicants, and apply the selection rule. <math>F(W, X, Y, Z) = \Sigma_m(4, 6, 7, 8, 12, 15)</math> <math>d(W, X, Y, Z) = \Sigma_m(2, 3, 5, 10, 11, 14)</math></p>	[6]
5.	<p>Optimize the following Boolean functions using K-map in (i) product-of-sums form, (ii) sum of products form <math>H(A, B, C, D) = \Pi_M(0, 2, 6, 7, 8, 9, 10, 12, 14, 15)</math></p>	[6]
6.	<p>Optimize the following expressions using K-map in (1) sum of products and (2) product of sums forms. Which one will you choose to implement the circuit diagram considering cost criteria? <math>G(A, B, C, D) = A\overline{C} + \overline{B}D + \overline{A}CD + ABCD</math></p>	[6]

## Answer Any One Question from Q7 and Q8

7.	<p>You have to design a combinational circuit that will take a 4-bit binary number as input and give output 1 if the number is <b>greater than 4 but less than 14</b>. You have to (i) find the simplified expression for the output bit in Sum-of-Products form, and (ii) draw the circuit diagram using basic gates.</p> <p>For example,</p> <div style="display: flex; justify-content: space-around;"> <div style="text-align: left;"> <p>a. Input: 0000, Output: 0 (Input &lt; 4)</p> <p>b. Input: 0100, Output: 0 (Input = 4)</p> </div> <div style="text-align: left;"> <p>c. Input: 1001, Output: 1 (Input &gt; 4)</p> <p>d. Input: 1110, Output: 0 (Input = 14)</p> </div> </div>	[6]
----	--	-----

8.	<p>You have to design a combinational circuit that will take a 4-bit binary number as input and give output 1 if the <b>number of '0's is even or equal to 3</b>. You have to (i) find the simplified expression for the output bit in Sum-of-Products form, and (ii) draw the circuit diagram using basic gates.</p> <p>For example,</p> <ul style="list-style-type: none"> <li>a. Input: 0110, Output: 1 (2 zeroes, even)</li> <li>b. Input: 1111, Output: 1 (0 zeroes, even)</li> <li>c. Input: 0001, Output: 1 (3 zeroes, 3)</li> <li>d. Input: 0111, Output: 0 (1 zeroes, odd)</li> </ul>	[6]
----	--	-----