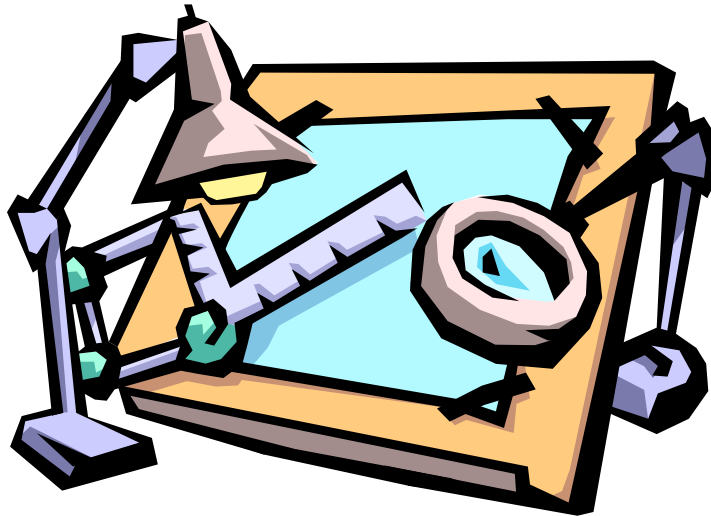


Sequential circuit design

- Now let's reverse the process: In **sequential circuit design**, we turn some description into a working circuit.
 - We first make a state table or diagram to express the computation.
 - Then we can turn that table or diagram into a sequential circuit.



Sequence recognizers

- A **sequence recognizer** is a special kind of sequential circuit that looks for a special bit pattern in some input.
- The recognizer circuit has only one input, X.
 - One bit of input is supplied on every clock cycle. For example, it would take 20 cycles to scan a 20-bit input.
 - This is an easy way to permit arbitrarily long input sequences.
- There is one output, Z, which is 1 when the desired pattern is found.
- Our example will detect the bit pattern "1001":

Inputs: 1 1 1 0 0 1 1 0 1 0 0 1 0 0 1 1 0 ...


Outputs: 0 0 0 0 0 1 0 0 0 0 0 1 0 0 1 0 0 ...

Here, one input and one output bit appear every clock cycle.

- This requires a sequential circuit because the circuit has to "remember" the inputs from previous clock cycles, in order to determine whether or not a match was found.

A basic state diagram

- What state do we need for the sequence recognizer?
 - We have to “remember” inputs from previous clock cycles.
 - For example, if the previous three inputs were 100 and the current input is 1, then the output should be 1.
 - In general, we will have to remember occurrences of parts of the desired pattern—in this case, 1, 10, and 100.
- We'll start with a basic state diagram (edges are labeled *input/output*):

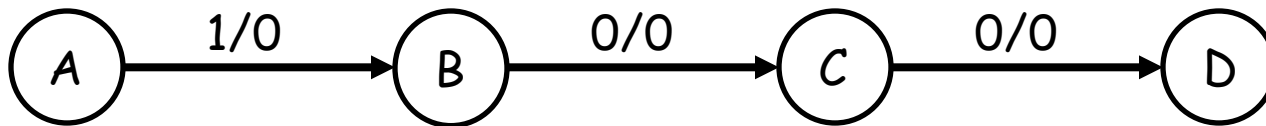


State	Meaning
A	None of the desired pattern (1001) has been input yet.
B	We've already seen the first bit (1) of the desired pattern.
C	We've already seen the first two bits (10) of the desired pattern.
D	We've already seen the first three bits (100) of the desired pattern.

Step 1: Making a state table

- The first thing you have to figure out is precisely how the use of state will help you solve the given problem.
 - Make a state table based on the problem statement. The table should show the present states, inputs, next states and outputs.
 - Sometimes it is easier to first find a state diagram and then convert that to a table.
- This is usually the most difficult step. Once you have the state table, the rest of the design procedure is the same for all sequential circuits.
- Sequence recognizers are especially hard! They're the hardest example we'll see in this class, so if you understand this you're in good shape.

A basic state diagram

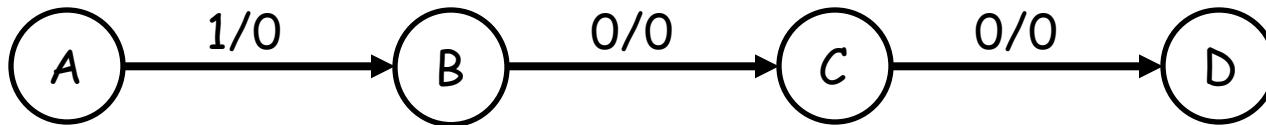
- What state do we need for the sequence recognizer?
 - We have to “remember” inputs from previous clock cycles.
 - For example, if the previous three inputs were 100 and the current input is 1, then the output should be 1.
 - In general, we will have to remember occurrences of parts of the desired pattern—in this case, 1, 10, and 100.
- We'll start with a basic state diagram:



State	Meaning
A	None of the desired pattern (1001) has been input yet.
B	We've already seen the first bit (1) of the desired pattern.
C	We've already seen the first two bits (10) of the desired pattern.
D	We've already seen the first three bits (100) of the desired pattern.

Overlapping occurrences of the pattern

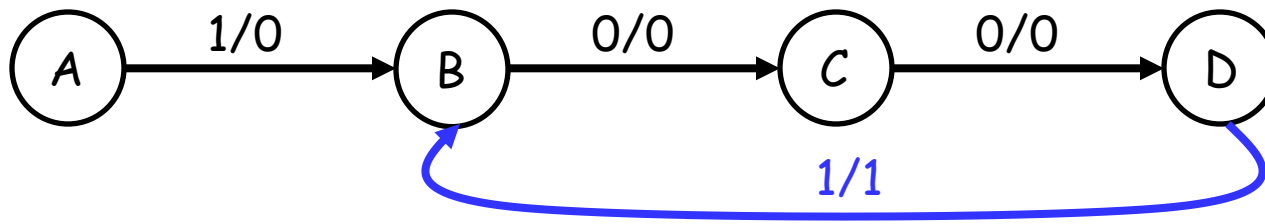
- What happens if we're in state D (the last three inputs were 100), and the current input is 1?
 - The output should be a 1, because we've found the desired pattern.
 - But this last 1 could also be the start of another occurrence of the pattern! For example, 100**1**001 contains *two* occurrences of 1001.
 - To detect overlapping occurrences of the pattern, the next state should be B.



State	Meaning
A	None of the desired pattern (1001) has been input yet.
B	We've already seen the first bit (1) of the desired pattern.
C	We've already seen the first two bits (10) of the desired pattern.
D	We've already seen the first three bits (100) of the desired pattern.


Filling in the other arrows

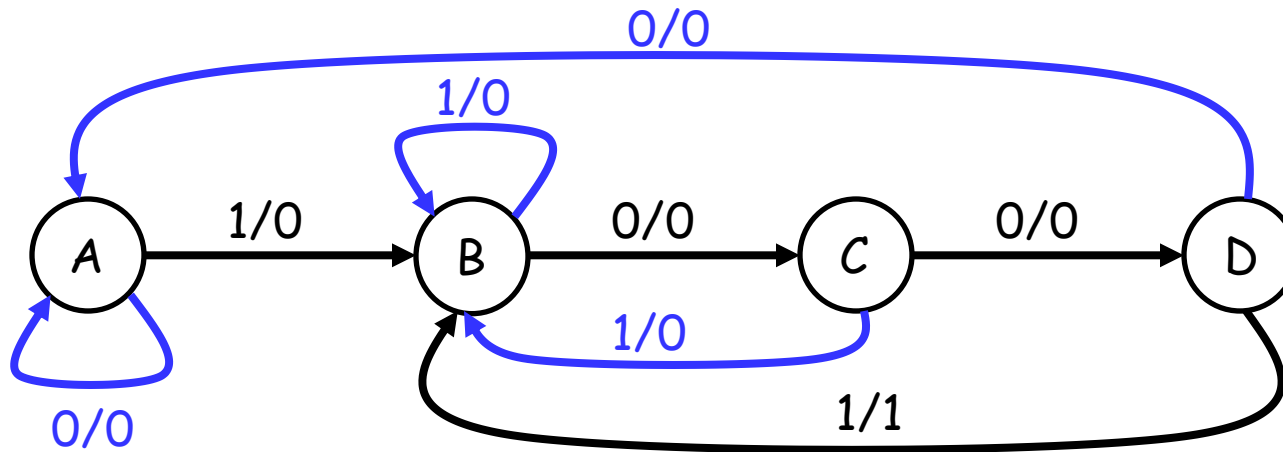- Remember that we need *two* outgoing arrows for each node, to account for the possibilities of $X=0$ and $X=1$.
- The remaining arrows we need are shown in blue. They also allow for the correct detection of overlapping occurrences of 1001.




State	Meaning
A	None of the desired pattern (1001) has been input yet.
B	We've already seen the first bit (1) of the desired pattern.
C	We've already seen the first two bits (10) of the desired pattern.
D	We've already seen the first three bits (100) of the desired pattern.

Finally, making the state table

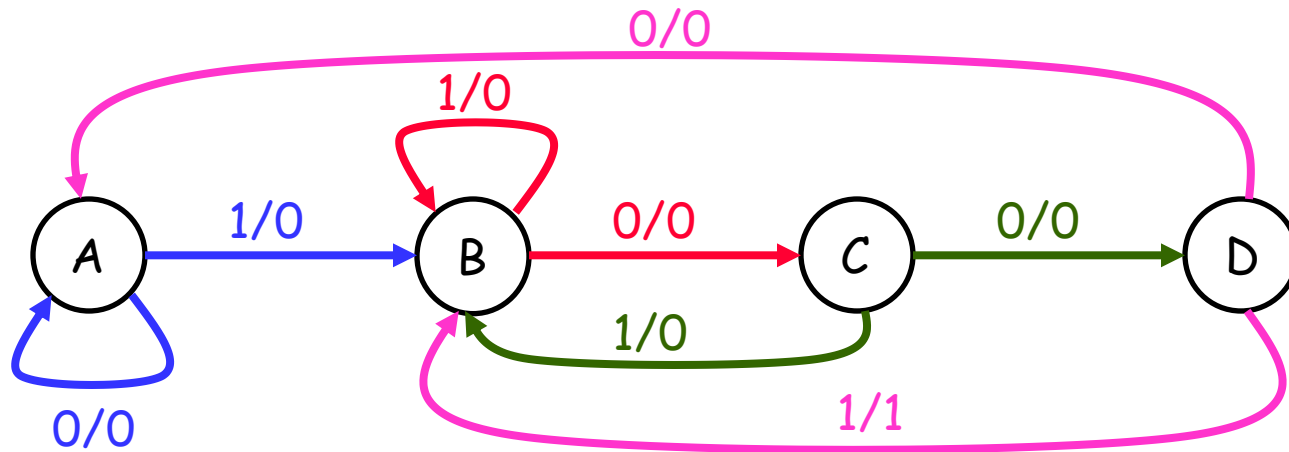

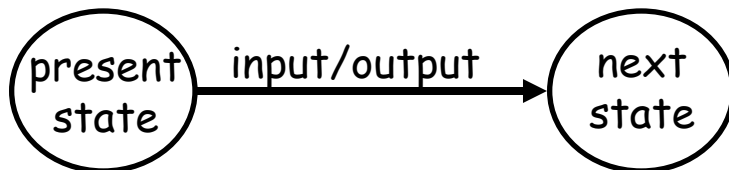Remember how the state diagram arrows correspond to rows of the state table:



Present State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	B	1

Sequential circuit design procedure

Step 1:

Make a state table based on the problem statement. The table should show the present states, inputs, next states and outputs. (It may be easier to find a state diagram first, and then convert that to a table.)

Step 2:

Assign binary codes to the states in the state table, if you haven't already. If you have n states, your binary codes will have at least $\lceil \log_2 n \rceil$ digits, and your circuit will have at least $\lceil \log_2 n \rceil$ flip-flops.

Step 3:

For each flip-flop and each row of your state table, find the flip-flop input values that are needed to generate the next state from the present state. You can use flip-flop excitation tables here.

Step 4:

Find simplified equations for the flip-flop inputs and the outputs.


Step 5:

Build the circuit!

Step 2: Assigning binary codes to states

- We have four states ABCD, so we need at least two flip-flops Q_1Q_0 .
- The easiest thing to do is represent state A with $Q_1Q_0 = 00$, B with 01, C with 10, and D with 11.
- The state assignment can have a big impact on circuit complexity, but we won't worry about that too much in this class.

Present State	Input	Next State	Output
A	0	A	0
A	1	B	0
B	0	C	0
B	1	B	0
C	0	D	0
C	1	B	0
D	0	A	0
D	1	B	1

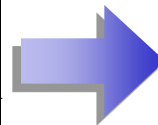

Present State		Input X	Next State		Output Z
Q_1	Q_0		Q_1	Q_0	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	1	1

Step 3: Finding flip-flop input values

- Next we have to figure out how to actually make the flip-flops change from their present state into the desired next state.
- This depends on what kind of flip-flops you use!
- We'll use two JKs. For each flip-flop Q_i , look at its present and next states, and determine what the inputs J_i and K_i should be in order to make that state change.

Present State		Input X	Next State		Flip flop inputs				Output Z
Q_1	Q_0		Q_1	Q_0	J_1	K_1	J_0	K_0	
0	0	0	0	0					0
0	0	1	0	1					0
0	1	0	1	0					0
0	1	1	0	1					0
1	0	0	1	1					0
1	0	1	0	1					0
1	1	0	0	0					0
1	1	1	0	1					1

Finding JK flip-flop input values

- For JK flip-flops, this is a little tricky. Recall the characteristic table:

J	K	$Q(t+1)$	Operation
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

- If the present state of a JK flip-flop is 0 and we want the next state to be 1, then we have *two* choices for the JK inputs:
 - We can use JK=10, to explicitly set the flip-flop's next state to 1.
 - We can also use JK=11, to complement the current state 0.
- So to change from 0 to 1, we must set J=1, but K could be *either* 0 or 1.
- Similarly, the other possible state transitions can all be done in two different ways as well.

JK excitation table


- An **excitation table** shows what flip-flop inputs are required in order to make a desired state change.

Q(t)	Q(t+1)	J	K	Operation
0	0	0	x	No change/reset
0	1	1	x	Set/complement
1	0	x	1	Reset/complement
1	1	x	0	No change/set


- This is the same information that's given in the characteristic table, but presented "backwards."

J	K	Q(t+1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement


Excitation tables for all flip-flops

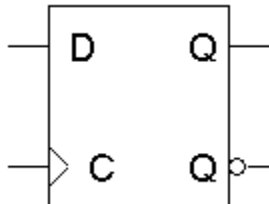

$Q(t)$	$Q(t+1)$	D	Operation
0	0	0	Reset
0	1	1	Set
1	0	0	Reset
1	1	1	Set

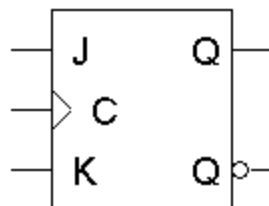

$Q(t)$	$Q(t+1)$	J	K	Operation
0	0	0	x	No change/reset
0	1	1	x	Set/complement
1	0	x	1	Reset/complement
1	1	x	0	No change/set

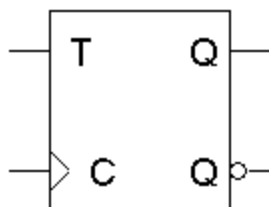

$Q(t)$	$Q(t+1)$	T	Operation
0	0	0	No change
0	1	1	Complement
1	0	1	Complement
1	1	0	No change

Back to the example

- We can now use the JK excitation table on the right to find the correct values for *each* flip-flop's inputs, based on its present and next states.

Q(t)	Q(t+1)	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Present State		Input X	Next State		Flip flop inputs				Output Z
Q ₁	Q ₀		Q ₁	Q ₀	J ₁	K ₁	J ₀	K ₀	
0	0	0	0	0					0
0	0	1	0	1					0
0	1	0	1	0					0
0	1	1	0	1					0
1	0	0	1	1					0
1	0	1	0	1					0
1	1	0	0	0					0
1	1	1	0	1					1

Back to the example

- We can now use the JK excitation table on the right to find the correct values for *each* flip-flop's inputs, based on its present and next states.

Q(t)	Q(t+1)	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Present State		Input X	Next State		Flip flop inputs				Output Z
Q ₁	Q ₀		Q ₁	Q ₀	J ₁	K ₁	J ₀	K ₀	
0	0	0	0	0	0	x	0	x	0
0	0	1	0	1	0	x	1	x	0
0	1	0	1	0	1	x	x	1	0
0	1	1	0	1	0	x	x	0	0
1	0	0	1	1	x	0	1	x	0
1	0	1	0	1	x	1	1	x	0
1	1	0	0	0	x	1	x	1	0
1	1	1	0	1	x	1	x	0	1

Step 4: Find equations for the FF inputs and output

- Now you can make K-maps and find equations for each of the four flip-flop inputs, as well as for the output Z.
- These equations are in terms of the present state and the inputs.
- The advantage of using JK flip-flops is that there are many don't care conditions, which can result in simpler MSP equations.

Present State		Input X	Next State		Flip flop inputs				Output Z
Q ₁	Q ₀		Q ₁	Q ₀	J ₁	K ₁	J ₀	K ₀	
0	0	0	0	0	0	x	0	x	0
0	0	1	0	1	0	x	1	x	0
0	1	0	1	0	1	x	x	1	0
0	1	1	0	1	0	x	x	0	0
1	0	0	1	1	x	0	1	x	0
1	0	1	0	1	x	1	1	x	0
1	1	0	0	0	x	1	x	1	0
1	1	1	0	1	x	1	x	0	1

$$J_1 = X' Q_0$$

$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$

$$K_0 = X'$$

$$Z = Q_1 Q_0 X$$


Step 5: Build the circuit

- Lastly, we use these simplified equations to build the completed circuit.

$$J_1 = X' Q_0$$
$$K_1 = X + Q_0$$

$$J_0 = X + Q_1$$
$$K_0 = X'$$

$$Z = Q_1 Q_0 X$$

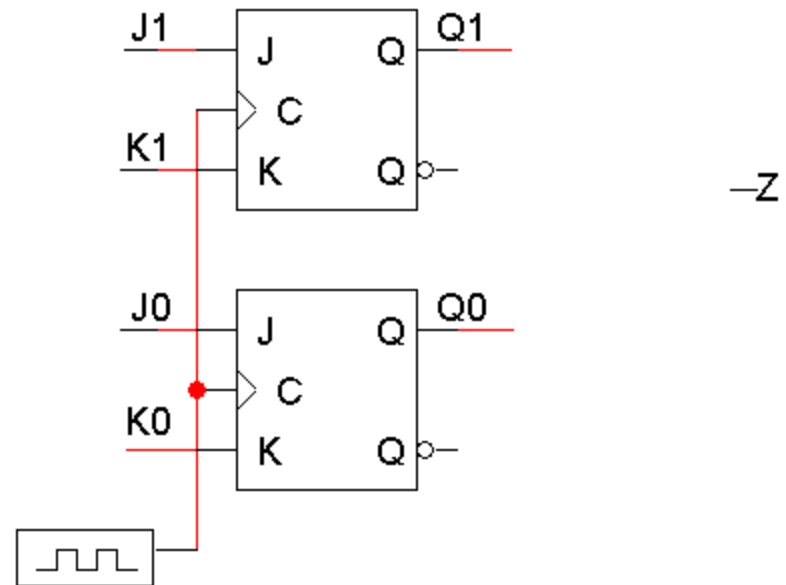


Step 5: Build the circuit

- Lastly, we use these simplified equations to build the completed circuit.

$$J_1 = X' Q_0$$
$$K_1 = X + Q_0$$


$$J_0 = X + Q_1$$
$$K_0 = X'$$

$$Z = Q_1 Q_0 X$$

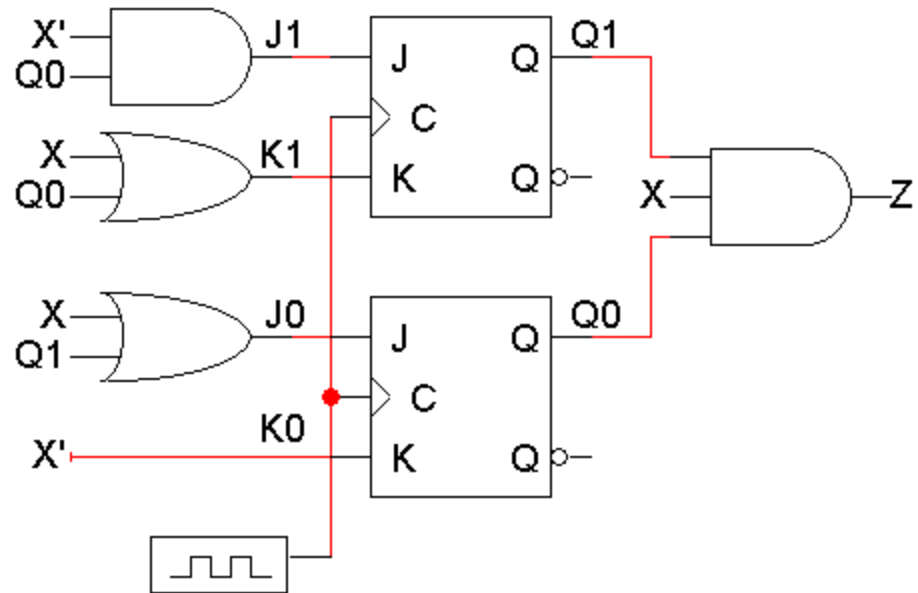

Timing diagram

- Here is one example timing diagram for our sequence detector.
 - The flip-flops Q_1Q_0 start in the initial state, 00.
 - On the first three positive clock edges, X is 1, 0, and 0. These inputs cause Q_1Q_0 to change, so after the third edge $Q_1Q_0 = 11$.
 - Then when $X=1$, Z becomes 1 also, meaning that 1001 was found.
- The output Z does not have to change at positive clock edges. Instead, it may change whenever X changes, since $Z = Q_1Q_0X$.

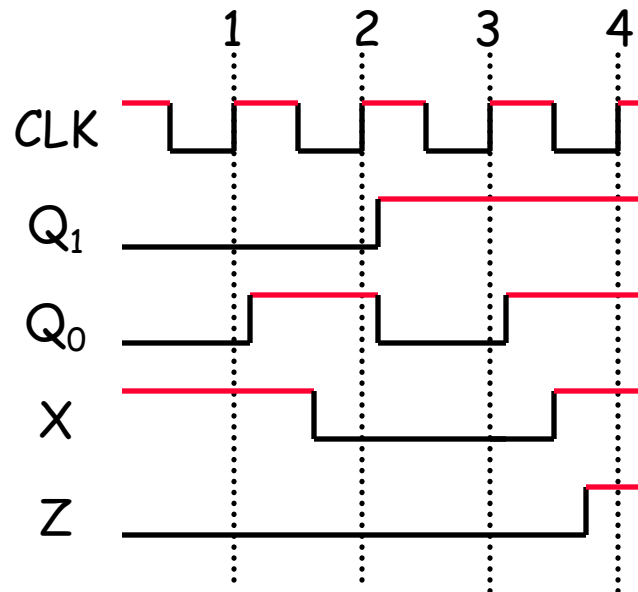

Building the same circuit with D flip-flops

- What if you want to build the circuit using D flip-flops instead?
- We already have the state table and state assignments, so we can just start from Step 3, finding the flip-flop input values.
- D flip-flops have only one input, so our table only needs two columns for D_1 and D_0 .

Present State		Input X	Next State		Flip-flop inputs		Output Z
Q_1	Q_0		Q_1	Q_0	D_1	D_0	
0	0	0	0	0			0
0	0	1	0	1			0
0	1	0	1	0			0
0	1	1	0	1			0
1	0	0	1	1			0
1	0	1	0	1			0
1	1	0	0	0			0
1	1	1	0	1			1

D flip-flop input values (Step 3)

- The D excitation table is pretty boring; set the D input to whatever the next state should be.
- You don't even need to show separate columns for D_1 and D_0 ; you can just use the Next State columns.

Q(t)	Q(t+1)	D	Operation
0	0	0	Reset
0	1	1	Set
1	0	0	Reset
1	1	1	Set

Present State		Input X	Next State		Flip flop inputs		Output Z
Q_1	Q_0		Q_1	Q_0	D_1	D_0	
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0
0	1	1	0	1	0	1	0
1	0	0	1	1	1	1	0
1	0	1	0	1	0	1	0
1	1	0	0	0	0	0	0
1	1	1	0	1	0	1	1

Finding equations (Step 4)

- You can do K-maps again, to find:


$$D_1 = Q_1 Q_0' X' + Q_1' Q_0 X'$$

$$D_0 = X + Q_1 Q_0'$$

$$Z = Q_1 Q_0 X$$

Present State		Input X	Next State		Flip flop inputs		Output Z
Q ₁	Q ₀		Q ₁	Q ₀	D ₁	D ₀	
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0
0	1	1	0	1	0	1	0
1	0	0	1	1	1	1	0
1	0	1	0	1	0	1	0
1	1	0	0	0	0	0	0
1	1	1	0	1	0	1	1


Building the circuit (Step 5)

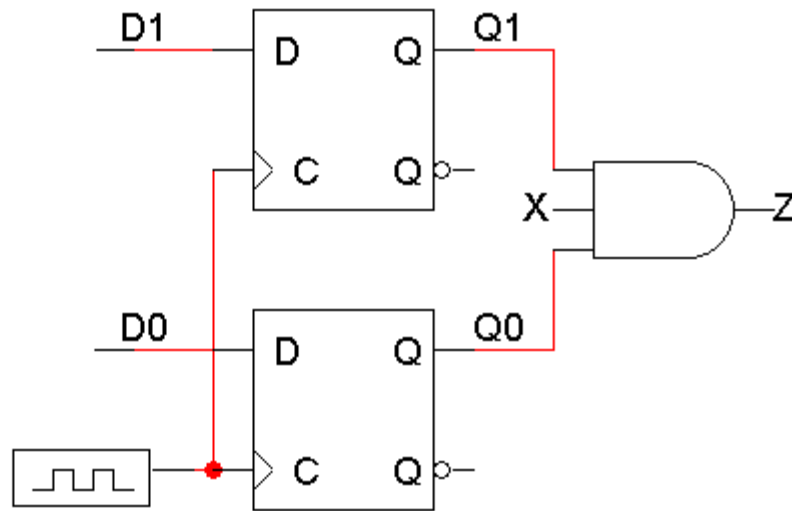


$$D1 = Q1 Q0' X' + Q1' Q0 X'$$

$$D0 = X + Q1 Q0'$$


Building the circuit (Step 5)

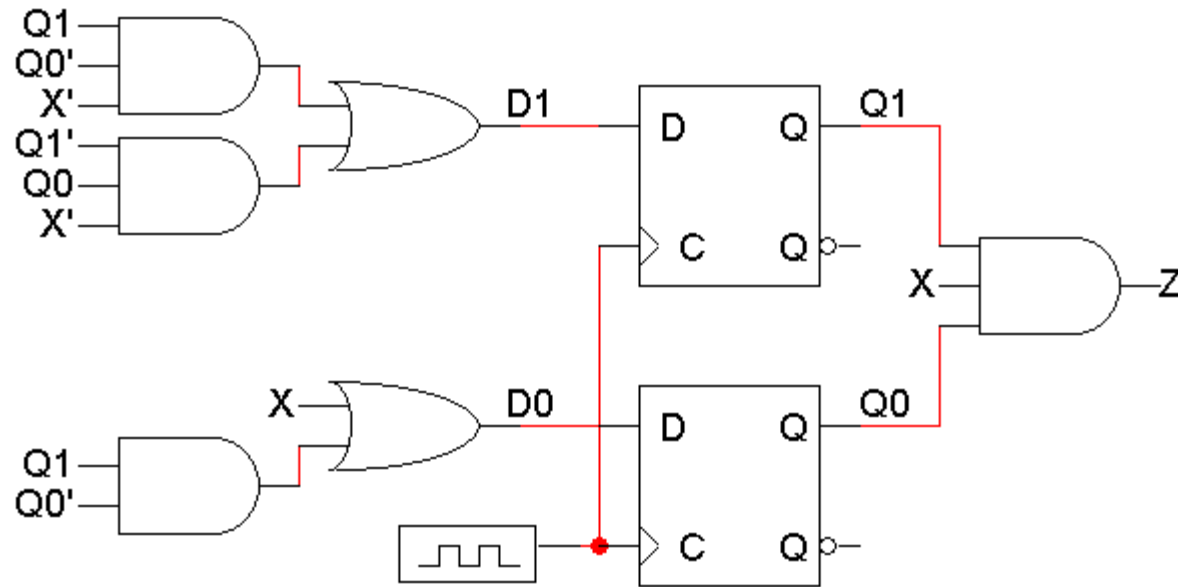


Flip-flop comparison

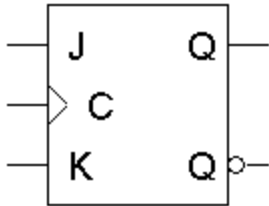

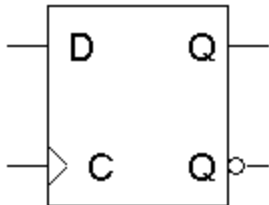JK flip-flops are good because there are many don't care values in the flip-flop inputs, which can lead to a simpler circuit.



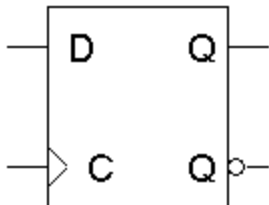D flip-flops have the advantage that you don't have to set up flip-flop inputs at all, since $Q(t+1) = D$. However, the D input equations are usually more complex than JK input equations



In practice, D flip-flops are used more often.

- There is only one input for each flip-flop, not two.
- There are no excitation tables to worry about.
- D flip-flops can be implemented with slightly less hardware than JK flip-flops.

An Aside On State Encoding

- You do not have to use the most *compact* encoding of states possible
- Here is another possibility: suppose you have four states A, B, C, D
 - Create one flip flop for each of A, B, C, D
 - Feed the Set and Reset lines of these flip-flops based on current state and inputs
 - This uses more flip-flops (4 instead of the minimum 2) but may result in a much simpler circuit overall
 - *The encoding and decoding of states is entirely artificial; it depends completely on the choice of state encodings. A little thinking about the circuit may lead you to a state encoding that simplifies the circuit a lot.*

Summary

- The basic sequential circuit design procedure:
 - Make a state table and, if desired, a state diagram. This step is usually the hardest.
 - Assign binary codes to the states if you didn't already.
 - Use the present states, next states, and flip-flop excitation tables to find the flip-flop input values.
 - Write simplified equations for the flip-flop inputs and outputs and build the circuit.
- Next, we'll look at common examples of sequential circuits, including different types of counters.