



United International University (UIU)
Department of Computer Science and Engineering
CSE 1325: DIGITAL LOGIC DESIGN, Final Summer 2023

Total Marks: **40** Duration: 2 hours

Answer ALL Questions

1.	<p>Implement a sequence recognizer using T or J-K flip-flops that can detect the “1010” subsequences, while overlap will be supported between detected subsequences.</p> <p>For this design:</p> <p>A. Draw the state diagram by using gray code for assigning state. [1.5]</p> <p>B. Draw the state table with output and Flip Flop inputs. [2]</p> <p>C. Minimize the functions of output and Flip Flop inputs. [2]</p> <p>D. Draw the circuit diagram using the block diagram of Flip Flops and basic gates. [1.5]</p> <p>E. For an input bit sequence of $x = \text{“101010001101001010”}$, what will be the output bit sequence? [1]</p>																
2.	<p>A. Design a 3-bit universal shift register with the functions given in the function table below. Here two control bits X and Y determine the mode of operation. Use D Flip Flops for your design. [6]</p> <table border="1" style="margin-left: auto; margin-right: auto;"><thead><tr><th>X</th><th>Y</th><th>Operation</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>Toggle</td></tr><tr><td>0</td><td>1</td><td>Parallel Load</td></tr><tr><td>1</td><td>0</td><td>Shift Right</td></tr><tr><td>1</td><td>1</td><td>Shift Left</td></tr></tbody></table> <p>B. Design a 4-bit asynchronous Downward Ripple Counter using negative edge J-K Flip Flops. [2]</p>	X	Y	Operation	0	0	Toggle	0	1	Parallel Load	1	0	Shift Right	1	1	Shift Left	
X	Y	Operation															
0	0	Toggle															
0	1	Parallel Load															
1	0	Shift Right															
1	1	Shift Left															
3.	<p>A sequential circuit has two D flip flops, one input X, and one output y is specified by the following input equations:</p> $A(t+1) = Ax \oplus B'x'$ $B(t+1) = (A' + B)x$ $y(t+1) = Ax' + (B' \oplus x)$ <p>A. Draw the logic diagram of the circuit. [2.5]</p> <p>B. Derive the state table. [3]</p> <p>C. Derive the state diagram. [2.5]</p>																
4.	<p>You are tasked with designing an alarm system for a security application. The system has multiple sensors: Door Sensor, Window Sensor, Motion Sensor, and Fire Sensor. Design a priority encoder circuit that detects the highest priority event among these sensors. Assume that Fire Sensor has the highest priority, followed by Motion Sensor, Door Sensor, and Window Sensor. [4]</p>																

5.	Design a 16:1 MUX using 4:1 MUX (as many as you require) only.	[4]
6.	Design an Octal to Binary Encoder. A. Draw the function table B. Write the equations for the output of your encoder. C. Draw the logic diagram of the encoder.	[4]
7.	Implement the following functions using a decoder and OR gates only. $F(X,Y,Z) = \prod M(0,3,5,6)$	[4]

Excitation Tables for different Flip-Flops

Q(t)	Q(t+1)	J	K	Operation
0	0	0	x	No change/reset
0	1	1	x	Set/complement
1	0	x	1	Reset/complement
1	1	x	0	No change/set

Q(t)	Q(t+1)	T	Operation
0	0	0	No change
0	1	1	Complement
1	0	1	Complement
1	1	0	No change